

28. Calculate: (FIG 9)

- a.  $L_{EQ}$ : \_\_\_\_\_
- b.  $L_T$ : \_\_\_\_\_
- c.  $X_{L1}$ : \_\_\_\_\_
- d.  $X_{LT}$ : \_\_\_\_\_
- e.  $X_{LEQ}$ : \_\_\_\_\_
- f.  $E_{LEQ}$ : \_\_\_\_\_
- g.  $E_{L1}$ : \_\_\_\_\_

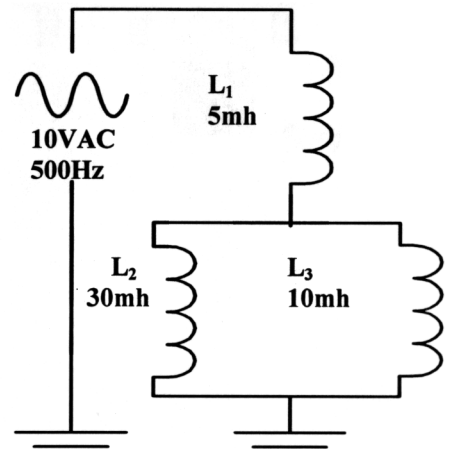


FIG 9

29. Calculate: (FIG 10)

- a.  $L_T$ : \_\_\_\_\_
- b.  $X_{LT}$ : \_\_\_\_\_
- c.  $R_T$ : \_\_\_\_\_
- d.  $Z$ : \_\_\_\_\_
- e.  $I_T$ : \_\_\_\_\_
- f.  $E_{R1}$ : \_\_\_\_\_
- g.  $E_{R2}$ : \_\_\_\_\_
- h.  $E_{L1}$ : \_\_\_\_\_
- $E_{L2}$ : \_\_\_\_\_

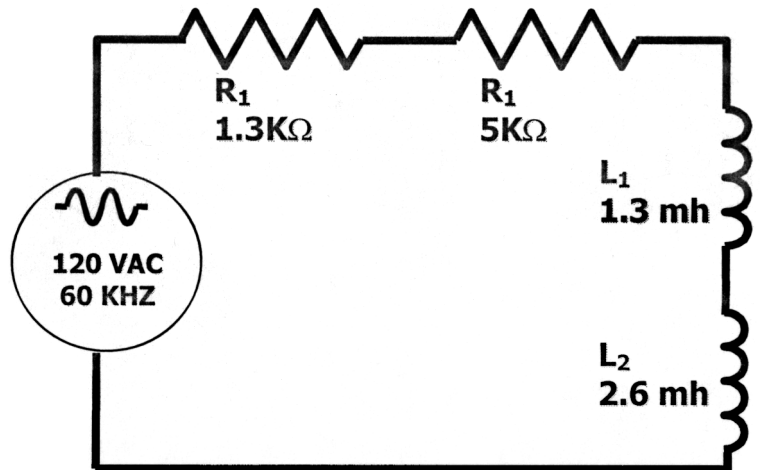


FIG 10

30. What is the phase relationship between voltage and current across an inductor?

31. What are the 3 parts of a capacitor?

32. (T or F) It matters how you place an electrolytic capacitor in a circuit?

33. What is the formula for capacitive reactance?